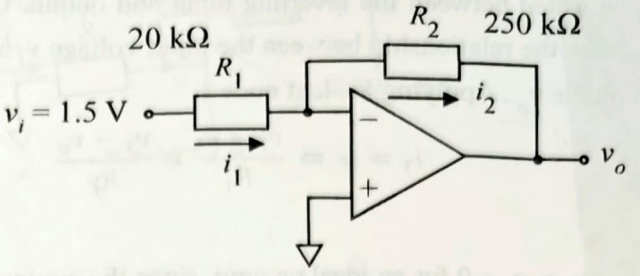
1. What is the output voltage v_o in the circuit , assuming an infinite open-loop gain A_O?



2. What input voltage v_i results in an output of 2 V in the circuit , assuming an open-loop gain $A_O = \infty$?

